

Experimenter's Corner

By Forrest M. Mims

PERCUSSION INSTRUMENT SYNTHESIZER

THANKS to John Simonton, and Don Lancaster, this magazine has featured articles on virtually every aspect of electronic music over the past several years.

Recently the electronic music bug bit me. Having tinkered with several of the basic circuits, I'm convinced that voicing circuits are by far the most challenging—and the most fun. Of course, they can be very difficult to implement, but the successful electronic synthesis of the unique "voice" or timbre of a particular musical instrument is quite rewarding.

Percussion instruments are among the simplest to simulate, so let's jump into electronic music by putting a per-

cussion synthesizer together. Since percussion instruments include the bell, gong, cymbals, triangle, xylophone, tambourine, and drum, a successful percussion synthesizer has lots of uses!

The first step of a successful design is to study the waveforms produced by the instrument to be synthesized. If you're new to electronic music, be prepared for a surprise! "Ordinary" musical instruments produce some very extraordinary waveforms. To make matters even worse, the amplitude (signal strength) of the waveform during the first 100 milliseconds or so is usually irregular and often unique. For example, the cello

has a gradual, slow amplitude rise time, but the tuba has a fast rise time in the form of a high-amplitude spike followed by the remainder of the sound "envelope." See Don Lancaster's article "Imitating Musical Instruments with Synthesized Sound" (POPULAR ELECTRONICS, August 1975, p. 37) for more information on the sound envelopes of these and other nonpercussion instruments.

Fortunately, percussion instruments produce a fairly orderly sound envelope. Figure 1 is a somewhat simplified version of the waveform

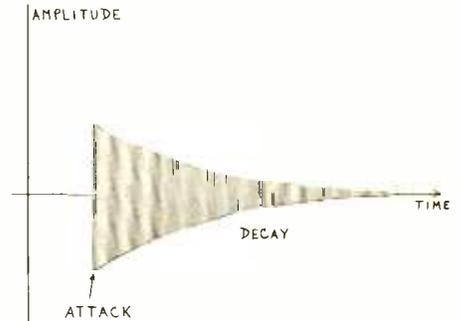


Fig. 1. In percussive waveform, rise is fast and decay slow.

produced by a typical percussion instrument. The waveform consists of a strong, fast rise-time "attack" followed by a gradual "decay." In the case of a bell, the attack is the initial high-amplitude sound produced when the bell is struck by its clapper. The decay is the ringing sound representative of the bell's natural resonant frequency.


Now that we've defined the frequency and amplitude relationships of the sounds we wish to simulate, we can start designing a circuit. Fortunately, our task is easy because "ringing," the effect we want to simulate, is a common and even pesky problem in many electronic circuits!

An active notch filter happens to make an excellent ringing circuit since it has a natural resonance frequency and can be adjusted to a critical point where oscillation can be externally stimulated and internally damped. As you may know, an active filter uses transistors or, better, one or more op amps to simulate a conventional filter. The active filter is superior to a passive filter since it has internal gain which replaces the losses of passive filters and since it can be made with a very high input impedance (very desirable) and a low output impedance (also very good).

NEW!
\$860


Announcing!! The world's most advanced, low cost, computer system available today!!

The MICRO-SPHERE 200

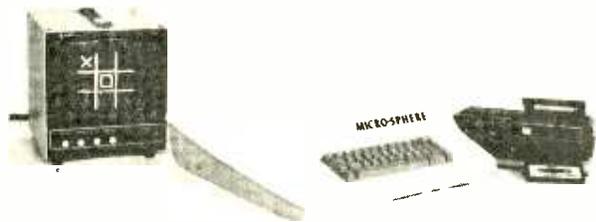

SPECIAL FEATURES:

- Completely Assembled and Tested (Ready to use; not a kit.)
- 4k RAM (EXPANDABLE TO 8k)
- CASSETTE LOADER
- Sphere Cassette Operating System (SCOS) supports file handling and Advanced Program Development, System, an aid for developing your programs.
- 16 Line by 21 Character Alpha Numeric Character Generator (128 by 128 B & W Dot Matrix Graphic System)
- Monte Carlo Games Package
- Operators Manual
- Attractive Mar-Resistant Plastic Case

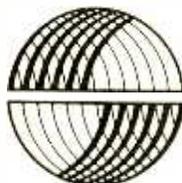

SPHERE CORPORATION

791 South 500 West Dept. 130 (801) 292-8466
Bountiful, Utah 84010


CIRCLE NO. 64 ON FREE INFORMATION CARD

ISO TIP

QUICK CHARGE

Recharges in 1/3rd the time of any other cordless iron.

Complete line of accessories available:

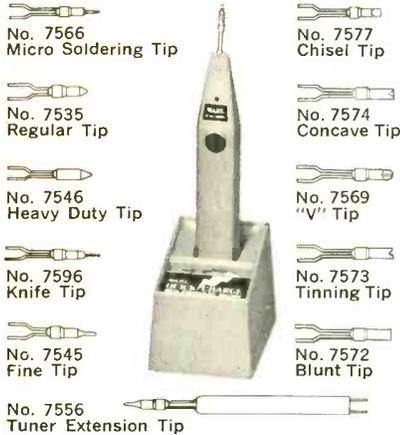

WAHL CLIPPER CORPORATION
 ORIGINATORS OF PRACTICAL CORDLESS SOLDERING
 Sterling, Illinois 61081 (815) 625-6525
 "Manufacturing Excellence Since 1919"

CIRCLE NO. 59 ON FREE INFORMATION CARD

ABOUT YOUR SUBSCRIPTION

Your subscription to POPULAR ELECTRONICS is maintained on one of the world's most modern, efficient computer systems, and if you're like 99% of our subscribers, you'll never have any reason to complain about your subscription service.

We have found that when complaints do arise, the majority of them occur because people have written their names or addresses differently at different times. For example, if your subscription were listed under "William Jones, Cedar Lane, Middletown, Arizona," and you were to renew it as "Bill Jones, Cedar Lane, Middletown, Arizona," our computer would think that two separate subscriptions were involved, and it would start sending you two copies of POPULAR ELECTRONICS each month. Other examples of combinations of names that would confuse the computer would include: John Henry Smith and Henry Smith; and Mrs. Joseph Jones and Mary Jones. Minor differences in addresses can also lead to difficulties. For example, to the computer, 100 Second St. is not the same as 100 2nd St.

So, please, when you write us about your subscription, be sure to enclose the mailing label from the cover of the magazine—or else copy your name and address exactly as they appear on the mailing label. This will greatly reduce any chance of error, and we will be able to service your request much more quickly.

MARCH 1976

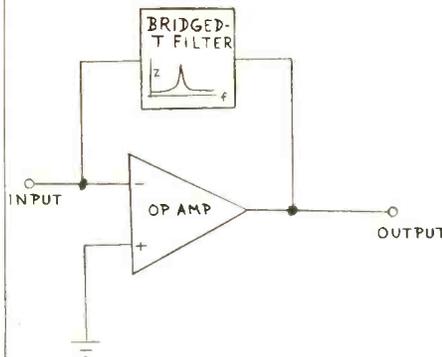


Fig. 2. Notch filter with maximum impedance at center frequency.

Figure 2 is the block diagram of a typical active notch filter which uses a single op amp, and Fig. 3 shows a working circuit. The filtering action takes place in the twin-T network formed by $R1$, $R2$, and their associated components. The twin-T notch filter is an old standby and is often used to block 60-Hz line noise in amplifiers and other circuits. The op amp provides restorative gain and interfacing to external circuits. You can operate the circuit as it is by connecting a miniature speaker to the output through a matching transformer (a unit with a 1000-ohm primary and an 8-ohm secondary), but you will have best results by connecting the circuit to an external audio amplifier.


The circuit works like this. The potentiometer is adjusted so that the filter just begins to oscillate and is then backed off until oscillation ceases. After this adjustment is made, a tiny input signal at pin 2 of the op amp will stimulate an oscillating attack followed by a gradual decay as the oscillation is dampened. How do you apply an input signal? Simple—just touch the touch plate (which can be a scrap of bare hookup wire) with a finger. The LM308, a precision op amp, has a typical input resistance of 40 megohms and readily accepts the small noise voltage from your body.

The frequency pattern of the circuit is very similar to Fig. 1, and the result is a very effective and realistic percussion simulator. You will probably have to make several adjustments of the pot for best results. If the circuit continues to oscillate without decaying, back off on the pot.

When $R1$ and $R2$ are about 100,000 ohms each, the circuit produces a very realistic bell sound when pin 2 is briefly touched. You can change the resonance frequency to simulate many other percussion instruments by

VIDEO PING PONG KITS

Tennis/Handball with on-screen scoring

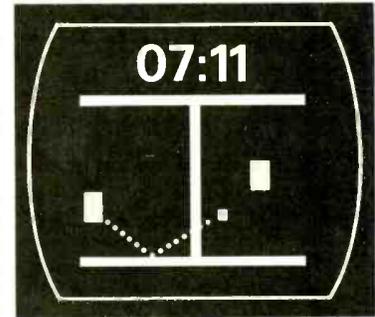

- Complete kit supplied, or any combination of plans, parts, PC board, etc.
- Anyone can build easily from concise instructions
- Attaches to TV antenna — no TV alterations required

IT'S THE HOTTEST ELECTRONIC GAME IN TOWN.

Send 50¢ for Info Pack—Refunded with Purchase.

INTERFAB
 27963 Cabot Road
 Laguna Niguel, California 92677 A

CIRCLE NO. 58 ON FREE INFORMATION CARD



LISTEN!

We're one of the country's largest Mail Order Houses of Stereo Equipment

Our volume buying power enables us to pass the savings on to you. Listen to us ... You can't go wrong.

Fill out this coupon and mail to address below for our latest Free Catalogs.

Name _____
 Address _____
 City _____
 State _____ Zip _____

AUDIO CATALOG

PE-3

STEREO DISCOUNTERS

7A AYLESBURY ROAD □ TIMONIUM, MD. 21093
 (301) 252-6880

CIRCLE NO. 54 ON FREE INFORMATION CARD 101

ALTAIR 8800 VIDEO TERMINAL

Video Interface. Plugs into the Altair or IMSAI 8800 bus and connects to standard TV monitor (or modified receiver). 8-bit input connects to almost any keyboard. Characters are displayed as 16 lines of 64 or 32 characters each, in a 7x9 dot matrix. (64 character line requires a high resolution monitor or extensively modified receiver.) The character set includes 128 upper and lower case ASCII characters and 64 graphics characters for plotting a 48x128 (or 64) grid. Characters are stored in the onboard memory and may be accessed directly by the computer. The output is standard 525 line EIA RS170 video.

\$160 Kit \$230 Assem. and tested (Add \$25 for 64 character option) delivery 30 days


Analog Interface. This board is a complete interface for a CRT graphics display or an X-Y plotter, and provides 8 channels of software-controlled A/D conversion. There are 1 or 2 channels of analog output with 10-bits resolution (0-10v or $\pm 5v$ out). 6-bits of latched digital output, and 8 analog comparators.

1 channel (0-10v) \$135 Kit \$175 Assem. and tested
2 channels (0-10v) \$185 Kit \$235 Assem. and tested
(Bipolar option ($\pm 5v$) add \$8 for 1 ch., \$12 for 2) delivery 30 days

Micro Computer. A one board computer system containing an 8080 processor, 512 bytes RAM, space for 1-3K bytes PROM or ROM, and a serial I/O port (optional). Compatible with IMSAI and Altair memory and peripherals. Supports multiprocessing. (Avail 1st Q. 1976)

Microcomputer System. A system based on our microcomputer and video boards. Includes motherboard, cabinet, power supply, and an operating system and monitor on PROM. (Avail 1st Q. 1976)

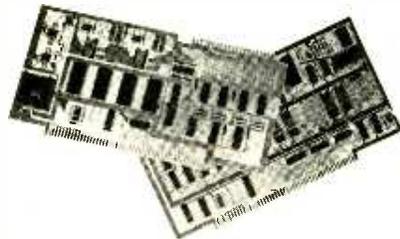All prices and specifications subject to change without notice. Prices are USA only - Calif. res. add 6% sales tax



POLYMORPHIC SYSTEMS
P.O. Box 2207, Goleta, California 93018

CIRCLE NO. 44 ON FREE INFORMATION CARD

A Major Advance...



- *EFFICIENT ENGINE PERFORMANCE
- *REDUCED MAINTENANCE EXPENSE
- *1 YEAR GUARANTEE OF PRODUCTS

For those who need maximum firing potential, Labtronics offers the Multiple Restrike Ignition. The system produces a high energy repetitive spark on each power stroke which insures the greatest statistical chance for proper ignition. Dependable system triggering from breaker-points, magnetic pick-ups or the extremely accurate '13A1-xx' infrared triggering unit. Order your system and enjoy the economy and peak performance of an efficient engine.

LABTRONICS, INCORPORATED

3635 HILLSIDE DRIVE • YPSILANTI, MICHIGAN 48197

MULTIPLE RESTRIKE SYSTEM		
[] Model VI	Programmable Duration	\$79.95
[] Model VI-B	Fixed Burst Duration	\$59.95
[] Model VI-C	Complete Optical System	\$79.95
HIGH ENERGY SYSTEM (Single Strike)		
[] Model V	Points Triggering System	\$29.95
[] Model V-C	Complete Optical System	\$47.95
TRIGGERING UNITS		
[] 13A1-xx	Optical Trigger Unit	\$24.95
[] 5129B	Magnetic Amplifier	\$ 4.95

CIRCLE NO. 29 ON FREE INFORMATION CARD

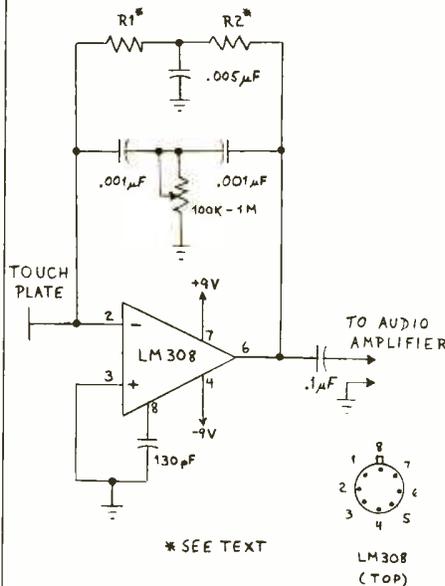


Fig. 3. Damped percussive waveform appears at filter output when touch plate is "struck."

changing R1 and R2. Of course you will have to readjust the pot to obtain the best voice for each instrument. Try these values for various effects:

Instrument	R1 and R2
Triangle	33K
Small bell	47K
Medium bell	150K
Large bell	470K
Drum	1M

A narrow tuning range will help you adjust the circuit for optimum voicing, so you will want to use as small a value for the pot as possible. If 100,000 isn't enough, use values of up to 1M.

Incidentally, you can use various op amps in this circuit, but they may not respond to a touch input signal. If this occurs, just connect a resistance of a few thousand ohms between the positive power-supply lead and pin 2 of the op amp through a momentary contact spst (normally open) pushbutton switch. Press the switch to ring the bell, strike the drum, or whatever. For a ding-dong effect, insert a small (about 0.001- μ F) capacitor in place of the resistor. Pressing the switch gives a sharp "ding" and releasing it gives a resonant "dong." This hookup makes a great doorbell circuit!

Finally, if this introductory project turns you on to electronic music, try building a complete percussion synthesizer from several filters adjusted to simulate various instruments. You can even build a realistic xylophone by building up a separate filter for each note.

SAVE!

MONEY • TIME • FREIGHT

- QUALITY STEREO EQUIPMENT AT LOWEST PRICES.
 - YOUR REQUEST FOR QUOTATION RETURNED SAME DAY.
 - FACTORY SEALED CARTONS—GUARANTEED AND INSURED.
 - SAVE ON NAME BRANDS LIKE:
- | | |
|--------|--------|
| A.D.C. | KLH |
| A.R. | SHURE |
| DYNACO | KOSS |
| SONY | FISHER |

PIONEER
AND MORE THAN 50 OTHERS
BUY THE MODERN WAY
BY MAIL—FROM

illinois audio

Department 217S
12 East Delaware
Chicago, Illinois 60611
312-664-0020

CIRCLE NO. 25 ON FREE INFORMATION CARD



12 REASONS YOUR CAR NEEDS TIGER CDI

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration and performance - Spark plugs last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - An Unconditional LIFETIME GUARANTEE Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back

TIGER 500 assembled \$53.95
TIGER SST assembled \$42.95
Post Paid in U.S.A.

Send check or money order with order to:

Tri-Star Corporation
P.O. Box 1727 C
Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED
CIRCLE NO. 55 ON FREE INFORMATION CARD

POPULAR ELECTRONICS